

# RTL CHALLENGE

**DAY – 13 :-** Today I Practiced Some problems based on Modules.

**Website used:-** HDL BITS

## Problem Statement:-

This instantiates a module of type mod\_a then Connects Module 3 pins (in1, in2, and out) to your top level module 3 ports (wire a, b, and out).

### Write your solution here

[Load a previous submission] ▼

Load

```
1 module top_module ( input a, input b, output out );
2     mod_a (.in1(a), .in2(b), .out(out));
3 endmodule
4 |
```

Submit


Submit (new window)

## Status: Success!

You have solved 2 problems. [See my progress...](#)
 
### Timing diagrams for selected test cases

These are timing diagrams from some of the test cases we used. They may help you debug your circuit. The diagrams show inputs to the circuit, outputs from your circuit, and the expected reference outputs. The "Mismatch" trace shows which cycles your outputs don't match the reference outputs (0 = correct, 1 = incorrect).



# RTL CHALLENGE

## Problem Statement:-

This problem is similar to the previous one. You are given a module named `mod_a` that has 2 outputs and 4 inputs, in that order. You must connect the 6 ports *by position* to your top-level module's ports `out1`, `out2`, `a`, `b`, `c`, and `d`, in that order.

You are given the following module:

```
module mod_a ( output, output, input, input, input, input );
```

## Write your solution here

[Load a previous submission]


```
1 module top_module (  
2     input a,  
3     input b,  
4     input c,  
5     input d,  
6     output out1,  
7     output out2  
8 );  
9     mod_a (out1,out2,a,b,c,d);  
10 endmodule  
11
```

## Status: Success!

You have solved 2 problems. [See my progress...](#)
 
## Timing diagrams for selected test cases

These are timing diagrams from some of the test cases we used. They may help you debug your circuit. The diagrams show inputs to the circuit, outputs from your circuit, and the expected reference outputs. The "Mismatch" trace shows which cycles your outputs don't match the reference outputs (0 = correct, 1 = incorrect).



# RTL CHALLENGE

## Problem Statement:-

This problem is similar to previous one . You are given a module named `mod_a` that has 2 outputs and 4 inputs, in some order. You must connect the 6 ports *by name* to your top-level module's ports:

```
module mod_a ( output out1, output out2, input in1, input in2, input in3, input in4);
```

## Write your solution here

[Load a previous submission]


```
1 module top_module (  
2     input a,  
3     input b,  
4     input c,  
5     input d,  
6     output out1,  
7     output out2  
8 );  
9     mod_a (.out1(out1), .out2(out2), .in1(a), .in2(b), .in3(c), .in4(d));  
10 endmodule  
11
```

## Status: Success!

You have solved 3 problems. [See my progress...](#)
 
## Timing diagrams for selected test cases

These are timing diagrams from some of the test cases we used. They may help you debug your circuit. The diagrams show inputs to the circuit, outputs from your circuit, and the expected reference outputs. The "Mismatch" trace shows which cycles your outputs don't match the reference outputs (0 = correct, 1 = incorrect).




# RTL CHALLENGE
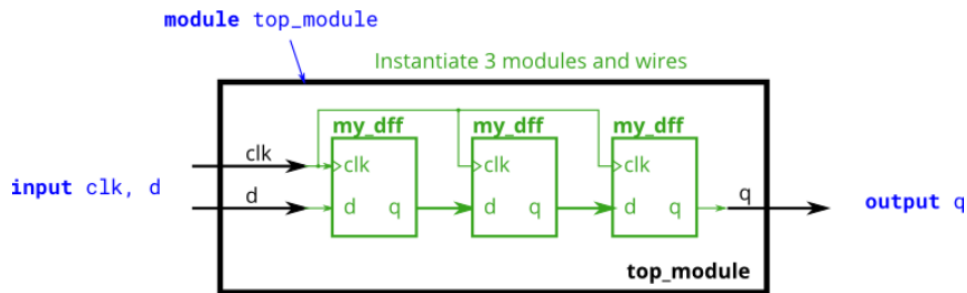
## Problem Statement:-

You are given a module `my_dff` with two inputs and one output (that implements a D flip-flop). Instantiate three of them, then chain them together to make a shift register of length 3. The `clk` port needs to be connected to all instances.

The module provided to you is: `module my_dff ( input clk, input d, output q );`



## Write your solution here

[Load a previous submission] ▼

Load

```
1 module top_module ( input clk, input d, output q );
2   wire w1,w2;
3   my_dff d1 (.clk(clk),.d(d),.q(w1));
4   my_dff d2 (.clk(clk),.d(w1),.q(w2));
5   my_dff d3 (.clk(clk),.d(w2),.q(q));
6 endmodule
7
```

Submit

Submit (new window)


## Status: Success!

You have solved 4 problems. [See my progress...](#)

## Timing diagrams for selected test cases

These are timing diagrams from some of the test cases we used. They may help you debug your circuit. The diagrams show inputs to the circuit, outputs from your circuit, and the expected reference outputs. The "Mismatch" trace shows which cycles your outputs don't match the reference outputs (0 = correct, 1 = incorrect).

### Shift register

 


# RTL CHALLENGE

## Problem Statement:-

This exercise is an extension of [module\\_shift](#). Instead of module ports being only single pins, we now have modules with vectors as ports, to which you will attach wire vectors instead of plain wires. Like everywhere else in Verilog, the vector length of the port does not have to match the wire connecting to it, but this will cause zero-padding or truncation of the vector. This exercise does not use connections with mismatched vector lengths.

You are given a module `my_dff8` with two inputs and one output (that implements a set of 8 D flip-flops). Instantiate three of them, then chain them together to make a 8-bit wide shift register of length 3. In addition, create a 4-to-1 multiplexer (not provided) that chooses what to output depending on `sel[1:0]`: The value at the input `d`, after the first, after the second, or after the third D flip-flop. (Essentially, `sel` selects how many cycles to delay the input, from zero to three clock cycles.)

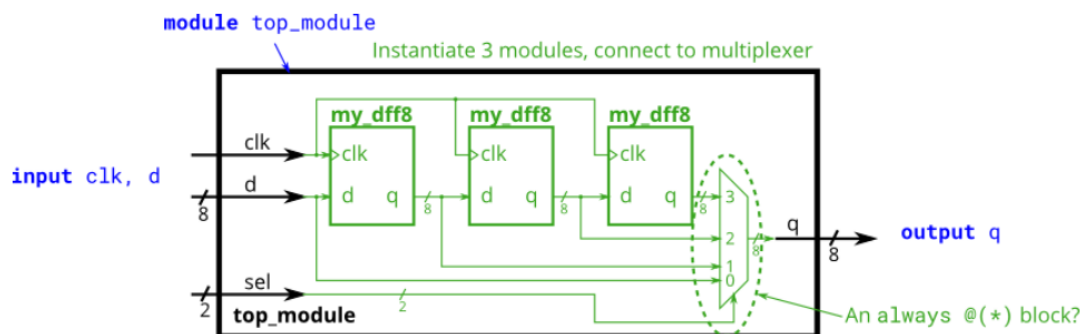The module provided to you is: `module my_dff8 ( input clk, input [7:0] d, output [7:0] q );`



# RTL CHALLENGE

## Write your solution here

[Load a previous submission] ▾

Load

```
1 module top_module (  
2     input clk,  
3     input [7:0] d,  
4     input [1:0] sel,  
5     output [7:0] q  
6 );  
7     wire [7:0] w1,w2,w3;  
8     my_dff8 d1 (.clk(clk), .d(d), .q(w1));  
9     my_dff8 d2 (.clk(clk), .d(w1), .q(w2));  
10    my_dff8 d3 (.clk(clk), .d(w2), .q(w3));  
11    always@(*)  
12    begin  
13        case (sel)  
14            2'b00: q=d;  
15            2'b01: q=w1;  
16            2'b10: q=w2;  
17            2'b11: q=w3;  
18        endcase  
19    end  
20 endmodule  
21
```

Submit

Submit (new window)

## Status: Success!

You have solved 5 problems. [See my progress...](#)

## Timing diagrams for selected test cases

These are timing diagrams from some of the test cases we used. They may help you debug your circuit. The diagrams show inputs to the circuit, outputs from your circuit, and the expected reference outputs. The "Mismatch" trace shows which cycles your outputs don't match the reference outputs (0 = correct, 1 = incorrect).

### Shift register

